

Analog Design Using g_m/I_d and f_t Metrics

Bernhard E. Boser


boser@eecs.berkeley.edu

Copyright © 2011 Bernhard Boser

Overview

- Traditional analog design methodologies typically require iteration
 - “Square Law” design equations are inaccurate for submicron devices
 - Depend on poorly defined parameters: μC_{ox} , V_{th} , V_{dsat} , ...
 - Difficult to achieve an “optimum” (e.g. minimum power)
- g_m/I_d -based design
 - Links design variables (g_m , f_t , I_d , ...) to specification (bandwidth, power)
 - Employs design charts to accurately size transistors

Motivation: A design example

 


Specifications:

- Small signal gain: $a_v = v_o/v_i = 5$
- Bandwidth: $B \geq 10\text{MHz}$
- Source resistance: $R_s = 1M\Omega$
- Load capacitance: $C_L = 5\text{pF}$
- Minimum power dissipation

Design Approaches

Design equations (Square-Law model)

 

$$I_d = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$


$$C_{GS} = C_{ox} WL$$

etc. ...


Difficulties

- Sub-micron transistors are not well described by these equations
- Non-obvious relation of model parameters to design specification
- Leads to many iterations
- What is the minimum power, anyway?


Natural Variables for Analog Design

 

 - Transconductance g_m
- Current I_d
- Efficiency g_m/I_d
- Capacitance C_{gs}, \dots
- Transit frequency $f_t = g_m/2\pi C_{gs}$



Example

 

Design constraints

- Low frequency gain

$$a_v = g_m R_L$$

- Pole at input

$$|p_{in}| = \frac{1}{R_s C_{gs}} \geq \frac{1}{2\pi B}$$

- Pole at output

$$|p_{out}| = \frac{1}{R_L C_L} \geq \frac{1}{2\pi B}$$

Specifications:

- Small signal gain: $a_v = v_o/v_i = 5$
- Bandwidth: $B \geq 10\text{MHz}$
- Source resistance: $R_s = 1\text{M}\Omega$
- Load capacitance: $C_L = 5\text{pF}$
- Minimum power dissipation

$$g_m \geq 2\pi B C_L$$

$$C_{GS} \leq \frac{1}{2\pi B R_s}$$

minimize I_d

Design Constraints and Objectives

Design constraints

$$g_m \geq 2\pi BC_L = 1.57 \text{ mS}$$

$$C_{GS} \leq \frac{1}{2\pi BR_s} = 16 \text{ fF}$$

minimize I_d

Design objectives

1. High current efficiency
to minimize power


$$\frac{g_m}{I_d}$$

2. Small $C_{gs} \rightarrow$ high f_T
to meet bandwidth
constraint

$$f_t = \frac{g_m}{2\pi C_{gs}}$$

Transit Frequency f_T

f_T versus g_m/I_d tradeoff

 

Compromise


- high g_m/I_d for low power
- high f_t for low C_{gs}

Design choice

- Maximum C_{gs} to meet specification at minimum power:
 - minimum f_t
 - minimum L
 - maximum g_m/I_d

$$f_{t,\min} = \frac{g_{m,\min}}{2\pi C_{gs,\max}} = \underline{\underline{15.7 \text{ GHz}}}$$

Transistor Current Efficiency g_m / I_d

 

- Strong Inversion
- Poor current efficiency
- Low output voltage range
- High f_t
- Small transistor

- Weak Inversion
- Good current efficiency (low V_d^{sat})
- High output voltage range
- Low f_t
- Large transistors


Completing the Design: Transistor Sizing

$$\frac{g_m}{I_d} = 14 \text{ V}^{-1} \text{ and } f_T = 16 \text{ GHz}$$





$$I_d = \frac{g_m}{g_m/I_d} = 112 \mu\text{A}$$

$$\frac{I_d}{W} = 12.4 \frac{\text{A}}{\text{m}} \quad (\text{from chart})$$

 
$$W = \frac{I_d}{I_d/W} = 9 \mu\text{m}$$



Verification: (1) Bias

    

Verification: (2) Specification

 

- Bias is as designed
- Gain and bandwidth slightly below spec
- Design ignored transistor r_o and self-loading
- Adjust by choosing a slightly higher f_t

Summary

Silicon

Complicated
Physics

SPICE Model

Complicated
Equations
(BSIM, PSP, ...)

**“Square Law”
based design**

Simple
“Square Law”
Equations

g_m/I_d
based design


g_m/I_d & f_t
Charts
(process specific)

- Accurate
- Good for verification
- Unsuitable for design


- Popular (textbooks)
- Poor accuracy
- Requires iterations
- Difficult to achieve optima

- Good accuracy
- Simple equations
- Transistor data from charts

NMOS Transit Frequency f_T

 


PMOS Transit Frequency f_T

 


Extrinsic Capacitances C_{gd} and C_{dd}


NMOS

 


PMOS

 


NMOS Current Density

 


PMOS Current Density

 


NMOS Intrinsic Gain $g_m r_o$

 


PMOS Intrinsic Gain $g_m r_o$

 

Intrinsic Gain $g_m r_o$

 

OTA Design Example



 


Specifications

- Voltage gain $A_v = 2$
- Dynamic range $DR \geq 72\text{dB}$
- Settling accuracy $\varepsilon_d \leq 100\text{ppm}$
- Settling time $t_s \leq 10\text{ns}$

- Switched capacitor gain stage (switches not shown)
- Applications: A/D converters, filters, ...

Circuit Topology

   


- Fully differential OTA
- Common mode and
- cascodes (for gain) not shown

- Differential mode half circuit
- Large & small signal models

Design Flow


1. Determine feedback factor
2. Determine C_L to meet dynamic range requirement
3. Determine g_m to meet settling requirement
4. Pick transistor characteristics based on analysis
 - Channel length L
 - Current efficiency g_m/I_D (or f_t)
5. Determine bias currents and transistor sizes
 - I_D (from g_m and g_m/I_D)
 - W (from I_D/W , current density chart)

(1) Feedback Factor

 

- Open feedback loop $\beta = \frac{v_x}{v_o} = \frac{C_f}{C_f + C_s + C_x} = \frac{1}{1 + A_v + \frac{C_x}{C_f}}$
- C_x is amplifier input capacitance ($C_{gs} + \dots$)
 - Small $C_x \rightarrow$ large feedback factor β
 - Large $C_x \rightarrow$ low transistor f_t requirement \rightarrow higher $g_m/I_d \rightarrow$ reduced current
 - Typically $C_x = (\frac{1}{3} \dots 1) \times (C_s + C_f)$ (shallow optimum)

(2) Dynamic Range

 

Output resistance: $R \approx \frac{1}{\beta g_{mn}}$

Noise density:

$$\frac{v_{o,n}^2}{\Delta f} = 4kT\gamma g_{mn} \left(1 + \frac{g_{mp}/I_d}{g_{mn}/I_d} \right) \cdot \left| \frac{R}{1 + j\omega RC_{Ltot}} \right|^2$$

PMOS

choose $\frac{g_{mp}}{I_d} < \frac{g_{mn}}{I_d}$ for low noise

Sampled noise: $\overline{v_{o,n}^2} = \frac{1}{\beta} \frac{kT}{C_{Ltot}} \gamma \left(1 + \frac{g_{mp}}{g_{mn}} \right)$

with $C_{Ltot} = C_L + (1 - \beta)C_f$



$$DR = \frac{\frac{1}{2} V_{o,max}^2}{v_{o,n}^2}$$

$$C_{Ltot} \geq 2kT \frac{\gamma}{\beta} \left(1 + \frac{g_{mp}}{g_{mn}} \right) \frac{DR}{V_{o,max}^2}$$

Dynamic range:

Minimum load capacitance:

(3) Settling

  

$$\text{Step response: } v_{out}(t) = V_{step} \frac{C_s}{C_f} \cdot \frac{T_0}{1+T_0} \cdot (1 - e^{-t/\tau}) \quad \text{with } \tau = \frac{C_{L\text{tot}}}{\beta g_{mn}}$$

ideal
response
static
error
dynamic
error

Solve for transconductance:

$$g_{mn} \geq -\frac{C_{L\text{tot}} \ln \varepsilon_d}{\beta t_s}$$

(4) Transistor Channel Length, g_m/I_d and f_t

	NMOS	PMOS	
L	180 nm	250 nm	$L_{n,min}$ reduces power
g_m/I_d	12 V^{-1}	8 V^{-1}	$g_{mp}/I_d < g_{mn}/I_d$ (noise)
f_t	19.7 GHz	3.78 GHz	$C_{gsn} < C_s + C_f$
I_d/W	18.7 A/m	7.06 A/m	

- Reduce g_m/I_d of NMOS if $C_{gsn} < C_s + C_f$
- f_t and I_d/W obtained from charts

(5) Bias Currents and Transistor Sizes

Specification

Dynamic range	DR := 6 · 12 dB	DR = 72	
Sampling rate	$f_s := 50\text{MHz}$	$t_s := \frac{1}{2 \cdot f_s}$	$t_s = 10\text{ns}$
Closed-loop gain	$A_{vo} := 2$		
Settling accuracy	$\epsilon := 2^{-13}$	$\epsilon = 122.07\text{ ppm}$	$\epsilon_d := 100\text{ppm}$
Supply voltage (min)	$V_{dd} := 1.8\text{V}$		
Sampling cap	$C_s := 200\text{fF}$	e.g. matching	$C_f := \frac{C_s}{A_{vo}}$

Design

Feedback factor: choose $C_x := \frac{C_s + C_f}{2}$ check below!

$$\beta := \frac{1}{1 + A_{vo} + \frac{C_x}{C_f}} \quad \beta = 0.222$$

Dynamic range: $V_{omax} := 0.6\text{V}$

$$C_{Ltot} := 2 \cdot k_B \cdot T_f \cdot \frac{1}{\beta} \cdot \left(1 + \frac{gm_idp}{gm_idn} \right) \cdot \frac{10^{0.1 \cdot DR}}{V_{omax}^2}$$

$$C_{Ltot} = 2.644\text{ pF}$$

Transistor L, gm/Id (Guess)

Channel length	$L_n := 180\text{nm}$	$L_p := 250\text{nm}$
gm/Id	$gm_idn := 12 \cdot V^{-1}$ $\frac{2}{gm_idn} = 166.667\text{ mV}$	$gm_idp := 8 \cdot V^{-1}$ $\frac{2}{gm_idp} = 250\text{ mV}$
current density (chart)	$id_wn := 18.7 \cdot \frac{A}{m}$	$id_wp := 7.06 \frac{A}{m}$
cutoff frequency (chart)	$f_{tn} := 19.7\text{GHz}$	$f_{tp} := 3.78\text{GHz}$

Transconductance:

$$\sqrt{v_{on}} = \sqrt{\frac{k_B \cdot T_f}{C_{Ltot}} \cdot \frac{1}{\beta} \cdot \left(1 + \frac{gm_idp}{gm_idn} \right)} = 106.57\text{ }\mu\text{V}$$

$$g_{mn} := \frac{C_{Ltot} \cdot \ln(\epsilon)}{\beta \cdot t_s} \quad g_{mn} = 10.721\text{ mS}$$

$$I_d := \frac{g_{mn}}{gm_idn} \quad I_d = 893.379\text{ }\mu\text{A}$$

$$C_{gsn} := \frac{g_{mn}}{2\pi \cdot f_{tn}} \quad C_{gsn} = 86.611\text{ fF} < C_x = 150\text{ fF}$$

ok!


Transistor sizing ...

$$W_n := \frac{I_d}{id_wn} \quad W_n = 47.774\text{ }\mu\text{m}$$


$$W_p := \frac{I_d}{id_wp} \quad W_p = 126.541\text{ }\mu\text{m}$$

Verification: (1) Test Bed


OTA

 

OTA in Feedback Loop

 


Verification: (2) Bias

 


So far, so good ...

Verification: (3) Dynamic Range

 


Verification: (4) Settling Time

 

- Dynamic settling error target met
- Large static error ~10%

Openloop Gain

 

- Openloop gain only $A_{vo} \sim 50$
- $T_o = \beta A_{vo} = 11$
- Add cascodes to increase low frequency gain

Generic g_m/I_d -based Design Flow

1. Determine g_m from design objectives (dynamic range, bandwidth, ...)
 2. Pick L
 - Short channel \rightarrow high f_t (high speed)
 - Long channel \rightarrow high intrinsic gain, good matching, ...
 3. Pick g_m/I_D or f_t
 - Large $g_m/I_D \rightarrow$ low power, large signal swing
 - Small $g_m/I_D \rightarrow$ high f_t (high speed)
 4. Determine I_D (from g_m and g_m/I_D)
 5. Determine W (from I_D/W , current density chart)
-
- Adapt to design specifics

Acknowledgements

- Prof. Boris Murmann
 - Prof. Paul Gray
 - Prof. Ali Niknejad
 - Prof. Elad Alon
-
- Many generations of students