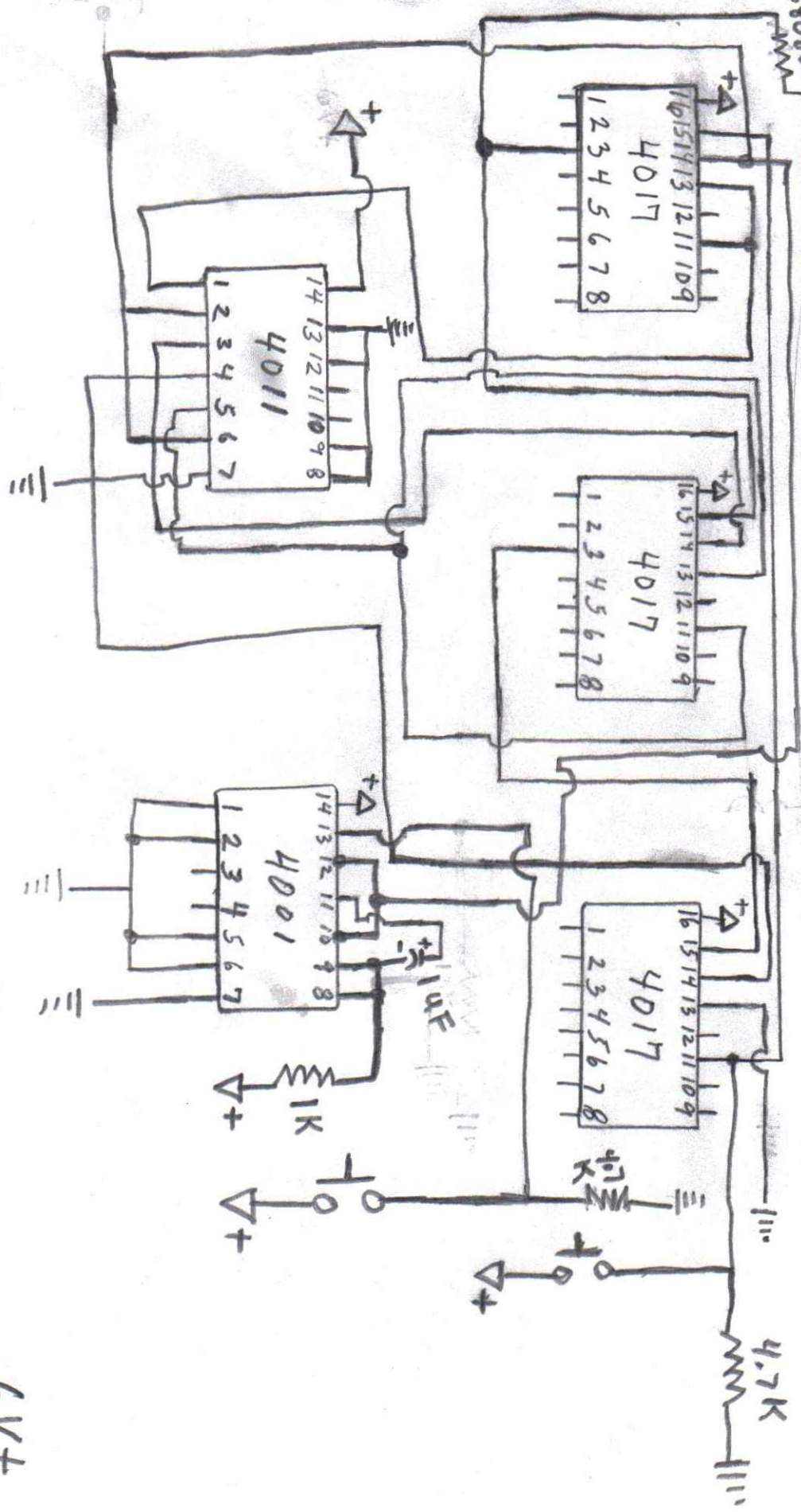


1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25



Each output 680  $\Omega$  Resistor to LED

6V+  
▽

1 - 4017

2 - 4017

3 - 4017

9 outputs

8 outputs

8 outputs