

Analysis of a Common Collector Circuit

These measurements were taken with a Fluke 85 multimeter on a Wisher-108 breadboard, the transistor used is a T2N3705 (2N3705) manufactured by Multicomp.

Initial Setup

The supply voltage (V_{CC}) is 5.22V DC with 2.4mV of 50Hz AC ripple.

R1 is a 1k Ω potentiometer set to 962 Ω .

R2 is a 4.7k Ω potentiometer set to 131.6 Ω .

Current Measurements

$I_B = 0.29\text{mA}$ approximately.

$I_E = 34.6\text{mA}$ approximately.

$I_C = 36.35\text{mA}$ approximately.

This give a total current gain (β) of 119.31 or 41.53 dB.

Voltage Measurements

$V_{CC} / V_{BB} = 5.22\text{V}$

$V_B = 4.95\text{V}$

$V_E = 4.19\text{V}$

$V_{BE} = 0.746\text{V}$

$V_{CE} = 1.024\text{V}$

The gives a total voltage gain (A_V) of 0.8464 or -1.4475 dB.

Derived Measurements

$V_{R1} = 278.98\text{mV}$

$R_E = 0.75144\Omega$ (This is the internal emitter resistance)

$Z_{in} = 89.654\Omega$

$Z_{out} = 0.75068\Omega$

Equations

$\beta = I_E / I_B$ or $20\log$ for dB

$A_V = V_E / V_B$ or $20\log$ for dB

$I_E = \beta * I_B$

$I_B = I_E / \beta$

$V_{R1} = I_B * R1$

$V_B = V_{BB} - V_{R1}$

$R_E = 26\text{mV} / I_E$

$Z_{in} = \beta * R_E$

$Z_{out} = Z_{in} / \beta$