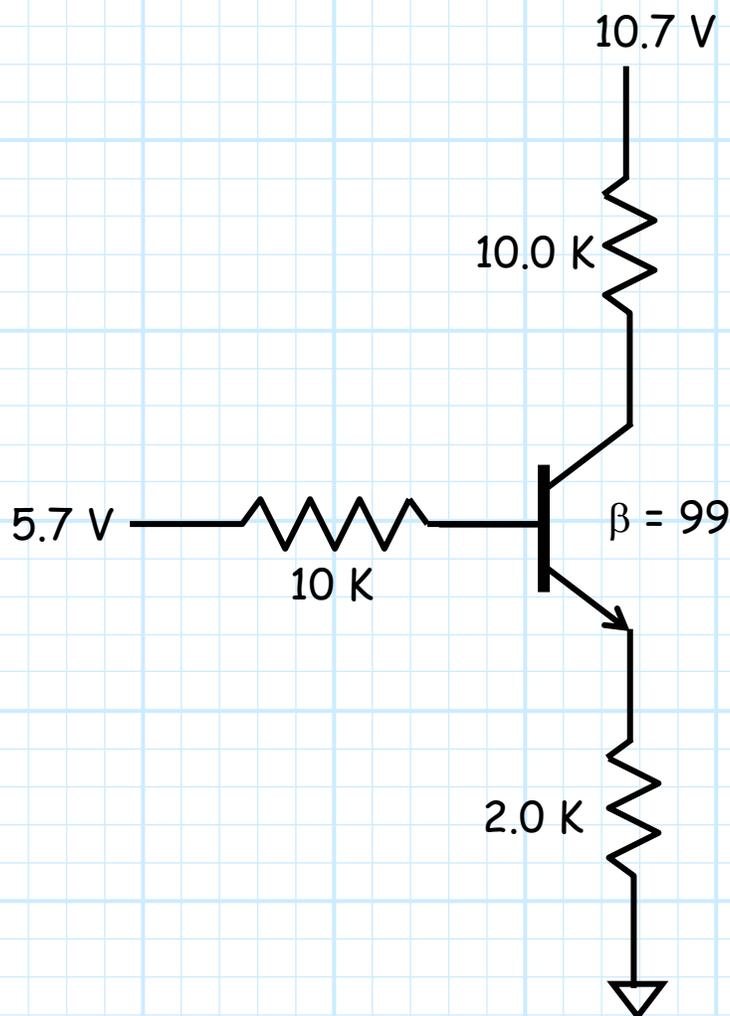


# Example: A BJT Circuit in Saturation

Determine all **currents** for the BJT in the circuit below.



*Hey! I remember this circuit, its just like a **previous example**. The BJT is in **active mode!***

Let's see if you are correct! **ASSUME** it is in active mode and **ENFORCE**  $V_{CE} = 0.7 \text{ V}$  and  $i_C = \beta i_B$ .

The B-E KVL is therefore:

$$5.7 - 10 i_B - 0.7 - 2 (99+1) i_B = 0$$

Therefore  $i_B = 23.8 \mu\text{A}$

*See! Base current  $i_B = 23.8 \mu A$ , just like before. Therefore collector current and emitter current are again  $i_C = 99i_B = 2.356 \text{ mA}$  and  $i_E = 100 i_B = 2.380 \text{ mA}$ . Right ?!*

Well **maybe**, but we still need to CHECK to see if our assumption is correct!

We know that  $i_B = 23.8 \mu A > 0$  ✓ , but what about  $V_{CE}$  ?

From collector-emitter KVL we get:

$$10.7 - 10 i_C - V_{CE} - 2 i_E = 0$$

Therefore,

$$V_{CE} = 10.7 - 10(2.36) - 2(2.38) = -17.66 \text{ V} < 0.7 \text{ V} \times$$

Our assumption is **wrong** ! The BJT is **not** in active mode.

In the previous example, the collector resistor was **1K** , whereas in this example the collector resistor is **10K**. Thus, there is 10X the **voltage drop** across the collector resistor, which **lowers** the collector voltage so much that the BJT cannot remain in the active mode.


**Q:** So what do we do now ?

**A:** Go to **Step 5**; change the assumption and try it again!

Lets ASSUME instead that the BJT is in **saturation**. Thus, we ENFORCE the conditions:

$$V_{CE} = 0.2 \text{ V} \quad V_{BE} = 0.7 \text{ V} \quad V_{CB} = -0.5 \text{ V}$$

Now lets ANALYZE the circuit !

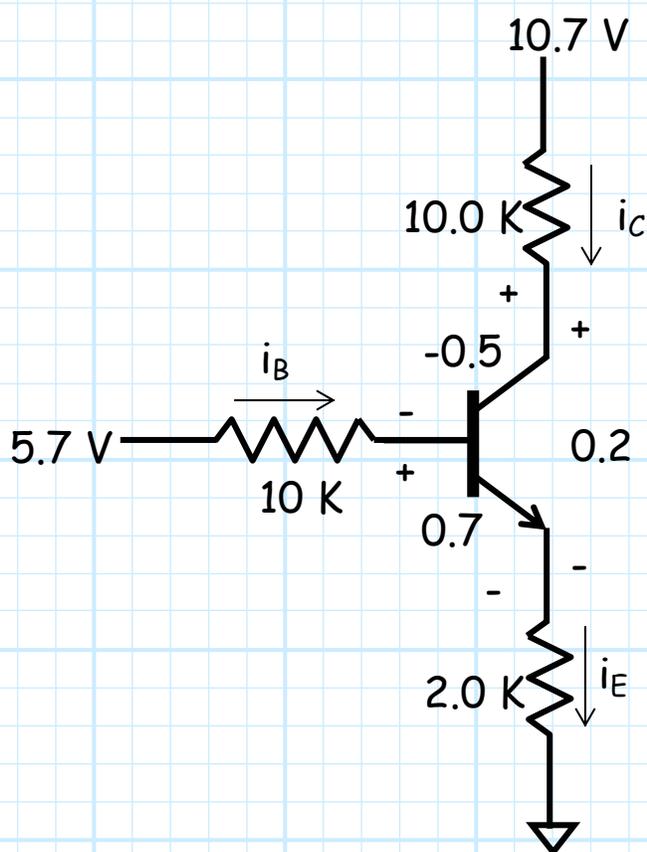

Note that we **cannot** directly determine the currents, as we **do not** know the base voltage, emitter voltage, or collector voltage.

But, we **do** know the **differences** in these voltages!

For example, we know that the collector voltage is 0.2 V **higher** than the emitter voltage, but we **do not** know what the collector or emitter voltages are!

**Q:** So, how the heck do we ANALYZE this circuit !?

**A:** Often, circuits with BJTs in **saturation** are somewhat more **difficult** to ANALYZE than circuits with **active** BJTs. There are often **many approaches**, but all result from a logical, systematic application of **Kirchoff's Laws!**

### ANALYSIS EXAMPLE 1 - Start with KCL

We know that  $i_B + i_C = i_E$  (KCL)

But, what **are**  $i_B$ ,  $i_C$ , and  $i_E$  ??


Well, from **Ohm's Law**:

$$i_B = \frac{5.7 - V_B}{10} \quad i_C = \frac{10.7 - V_C}{10} \quad i_E = \frac{V_E - 0}{10}$$

Therefore, combining with KCL:

$$\frac{5.7 - V_B}{10} + \frac{10.7 - V_C}{10} = \frac{V_E}{10}$$

Look what we have, **1 equation** and **3 unknowns**.

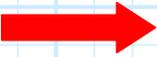 We need **2 more independent equations** involving  $V_B$ ,  $V_C$ , and  $V_E$ !

**Q:** *Two more independent equations !? It looks to me as if we have written all that we can about the circuit using Kirchoff's Laws.*

**A:** True! There are no more **independent** circuit equations that we can write using KVL or KCL ! But, recall the hint sheet:

*"Make sure you are using **all** available information".*

There is more **information** available to us - the ENFORCED conditions!

$$V_{CE} = V_C - V_E = 0.2 \quad \rightarrow \quad V_C = V_E + 0.2$$

$$V_{BE} = V_B - V_E = 0.7 \quad \rightarrow \quad V_B = V_E + 0.7$$

**Two more independent** equations! Combining with the earlier equation:

$$\frac{5.7 - (0.7 + V_E)}{10} + \frac{10.7 - (0.2 + V_E)}{10} = \frac{V_E}{10}$$


**One** equation and **one** unknown ! Solving, we get  $V_E = 2.2 \text{ V}$ .

**Inserting** this answer into the above equations, we get:

$$V_B = 2.9 \text{ V} \quad V_C = 2.4 \text{ V}$$

$$i_C = 0.83 \text{ mA} \quad i_B = 0.28 \text{ mA} \quad i_E = 1.11 \text{ mA}$$

## ANALYSIS EXAMPLE 2 - Start with KVL

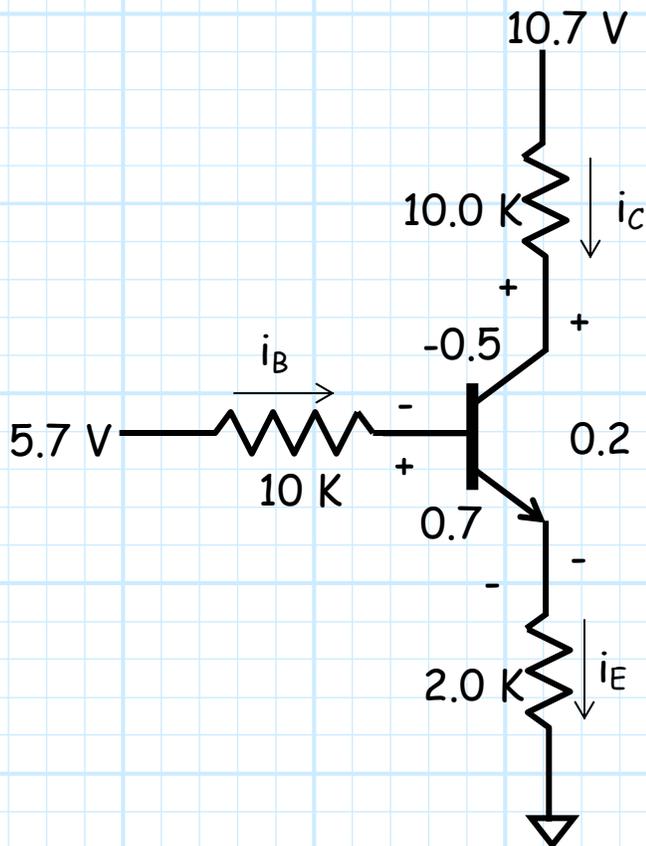

We can write the KVL equation for any **two** circuit legs:

B-E KVL:

$$5.7 - 10 i_B - 0.7 - 2 i_E = 0.0$$

C-E KVL:

$$10.7 - 10 i_C - 0.2 - 2 i_E = 0.0$$

Note the ENFORCED conditions are **included** in these KVL equations.

Simplifying, we get these 2 equations with 3 unknowns:

$$5.0 = 10 i_B + 2 i_E$$

$$10.5 = 10 i_C + 2 i_E$$

We need **one more** independent equation involving  $i_B$ ,  $i_C$ , and  $i_E$ .

Try KCL!

$$i_B + i_C = i_E$$

**Inserting** the KCL equation into the 2 KVL equations, we get:

$$5.0 = 12 i_B + 2 i_C$$

$$10.5 = 2 i_B + 12 i_C$$

Solving, we get the **same answers** as in analysis example 1.

**Lesson:** There are **multiple** strategies for analyzing these circuits; use the ones that you feel most **comfortable** with!

However you **ANALYZE** the circuit, you **must** in the end also **CHECK** your results.

First **CHECK** to see that **all** currents are **positive**:

$$i_C = 0.83 \text{ mA} > 0 \quad \checkmark \quad i_B = 0.28 \text{ mA} > 0 \quad \checkmark \quad i_E = 1.11 \text{ mA} > 0 \quad \checkmark$$

Also **CHECK** **collector current**:

$$i_C = 0.83 \text{ mA} < \beta i_B = 27.7 \text{ mA} \quad \checkmark$$

Our solution is **correct** !!!