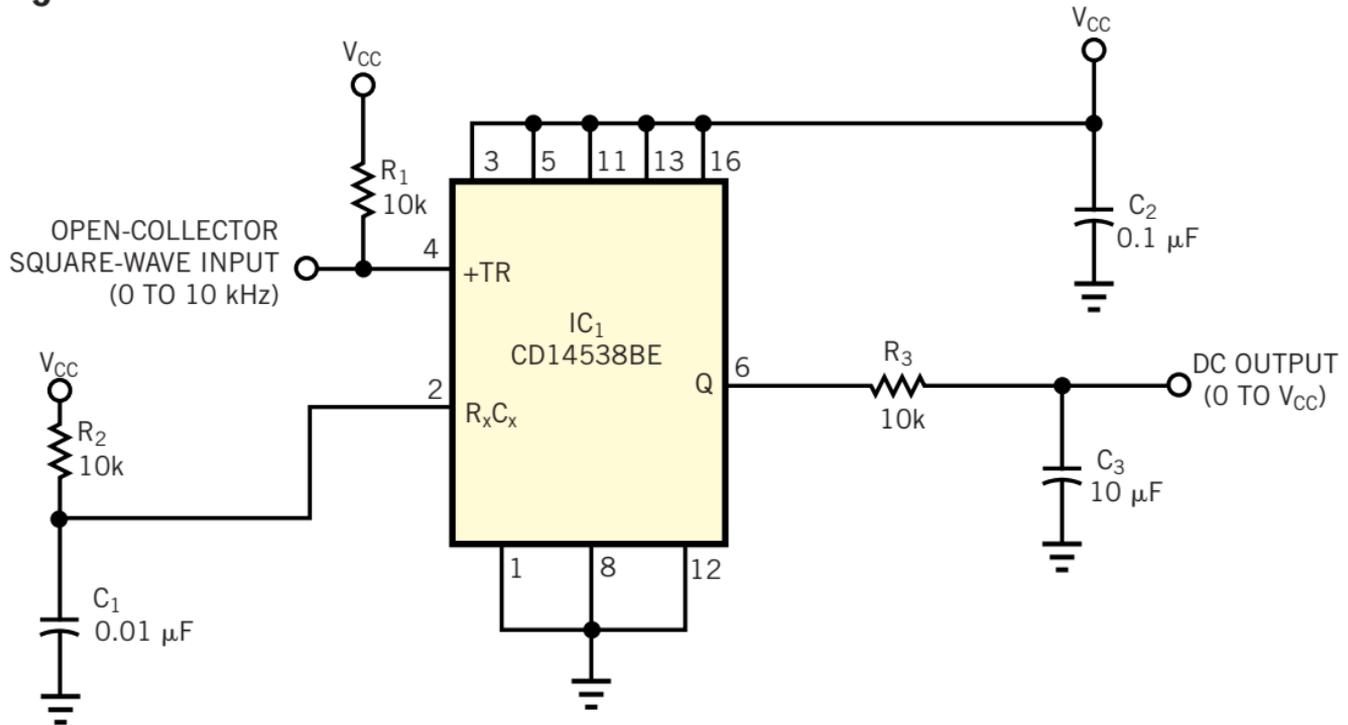


**Figure 1**



**A single CMOS one-shot multivibrator provides a simple and inexpensive frequency-to-voltage conversion function.**