



Q1 = 2N4230, 2N3906 or similar high-beta PNP transistor
 Select $R_X = [(V_S - 3V)/3V] \times 10 \text{ k}\Omega$

*Use stable components with low temperature coefficients