

## 2. Frequency analysis of transistor amplifiers


A. For circuit (a) below, calculate:

$R_e$  and  $R_c$  to make  $I_C \approx 0.2 \text{ mA}$  and  $V_{CE} \approx 6\text{V}$ .

$C_e$  to give a pole frequency at about 400 Hz, and  $C_c$  to give a pole at about 50 Hz.

The oscilloscope input resistance is  $1 \text{ M}\Omega$ . For initial calculations assume  $C_{\mu} = 5 \text{ pF}$  and  $C_{\text{CRO} + \text{cable}} = 110 \text{ pF}$ . (These will be measured in the lab.) The generator resistance is  $50 \Omega$ , which may be taken as a good approximation to zero for this experiment. Moreover, the input will be monitored across the generator and its voltage kept constant, so it may be treated as an ideal voltage source.

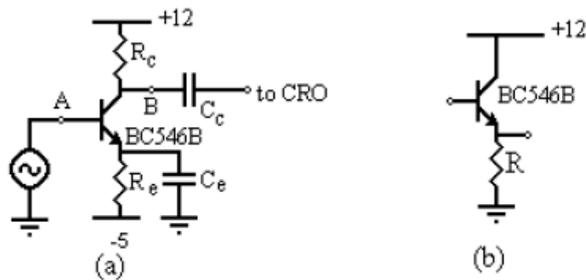Estimate the voltage gain, the frequency of the zero introduced by  $C_e$ , and the upper 3-dB frequency  $f_H$ . What is the voltage gain if  $C_e$  is omitted?



B. Circuit (b) is to be inserted in series at point B to buffer the load capacitance. Calculate  $R$  to give a collector current of about  $1.2 \text{ mA}$ . Assuming a 'typical' value for  $h_{fe}$ , recalculate  $f_H$ . Is the pole frequency introduced by  $C_c$  significantly affected?

C. Leaving circuit (b) in place, a  $10 \text{ k}\Omega$  resistor is inserted at point A (simulating a higher source resistance than that of the generator). Recalculate  $f_H$ . Is the pole frequency introduced by  $C_e$  affected?