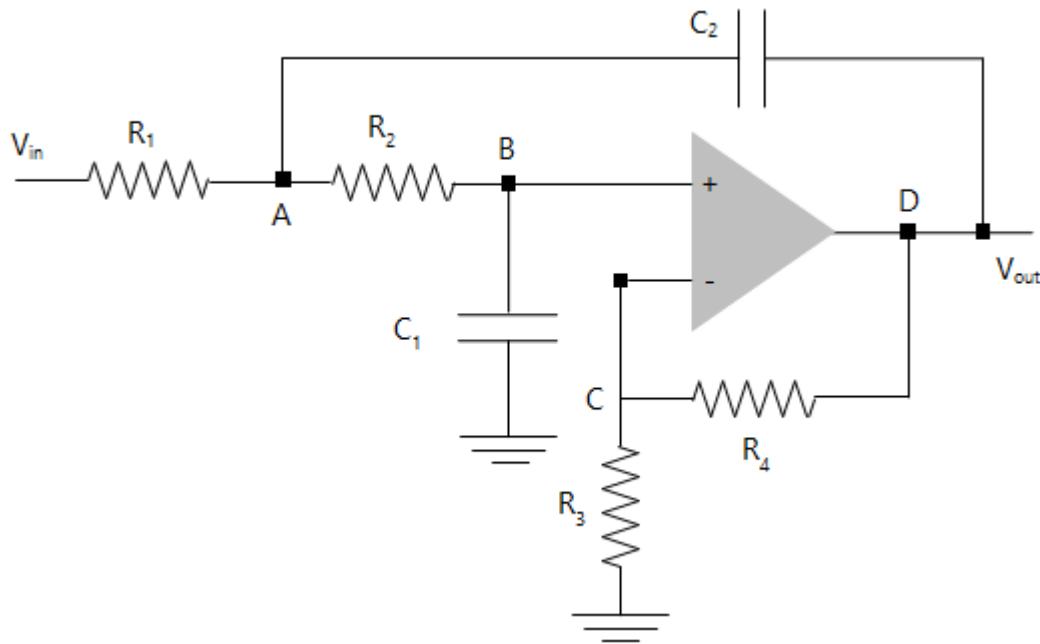




Sensitivity Analysis of a Sallen-Key Low-Pass Filter

This application performs a worst case circuit analysis of this filter circuit.



Specifically, the application

- derives a transfer function describing the ratio of the output voltage to the input voltage
- for each component, calculates the partial derivatives of the transfer function
- generates two parameter sets, taking into account the sign of the partial derivatives
- for both parameter sets, plots the DC response, response at 1.5 kHz, and a magnitude plot

Op amp parameters are taken from a data sheet for a ISL70444SEH op amp. The DC gain is 90 dB, so the open loop voltage gain A_{o1} is $10^{90/20} = 31623$

Parameters

The elements in this matrix contain the

- name of each component
- nominal parameter value
- lower tolerance value
- higher tolerance value

Resistors have a symmetric tolerance of 2%. Capacitors have an asymmetric tolerance of -19% to +15%.

	R_1	13.3×10^3	-0.02	0.02
	R_2	41.2×10^3	-0.02	0.02
	R_3	10×10^3	-0.02	0.02
	R_4	56.9×10^3	-0.02	0.02
	C_1	0.0068×10^{-6}	-0.19	0.15
	C_2	0.0068×10^{-6}	-0.19	0.15
data :=	R_{in}	10×10^3	0	0
	R_o	60	0	0
	A_{o1}	31623	0	0
	i_b	650×10^{-9}	-1	1
	i_{os}	50×10^{-9}	-1	1
	V_{os}	0.5×10^{-3}	-1	1

data := convert(data, listlist)

Circuit Analysis

Apply Kirchoff's Current Law

$$eqIA := \frac{V_A - V_{in}}{R_1} + (V_A - V_D) \cdot C_2 \cdot s + \frac{V_A - V_B}{R_2} = 0$$

$$eqIB := \frac{V_B - V_A}{R_2} + V_B \cdot C_1 \cdot s + i_{os} - i_b = 0$$

$$eqIC := \frac{V_C}{R_3} + \frac{V_C - V_D}{R_4} - i_b - i_{os} + \frac{V_C - V_{os} - V_B}{R_{in}} = 0$$

$$eqID := \frac{V_D - V_C}{R_4} + \frac{V_D - A_{o1} \cdot (V_C - V_{os} - V_B)}{R_o} + (V_D - V_A) \cdot C_2 \cdot s = 0$$

Symbolically solve for V_{out} in terms of V_{in}

sol := solve([eqIA, eqIB, eqIC, eqID], [V_A, V_B, V_C, V_D])

V_{out} := rhs(sol[1, 4])

Partial Derivatives of Output Voltage wrt Components

Generate a list of component names

```
varNames := [data[ .., 1][ ], s, Vin] = [R1, R2, R3, R4, C1, C2, Rin, Ro, Aol, ib, ios, Vos, s, Vin]
```

Generate a list of component nominal values

```
varValues := [data[ .., 2][ ], 1, 0]
```

Generate a list of equations for the component nominal values

```
values_eq := [seq(varNames[i] = varValues[i], i = 1..14)]
```

Hence the partial derivatives with respect to each component, evaluated at the nominal value.

```
derivs := [seq(eval(diff(Vout, varNames[j])), values_eq), j = 1..14)]
```

If the partial derivative is positive, V_{out} increases if the component value increases. However, if the partial derivative is negative, V_{out} decreases if the component value increases.

Hence a combination of the lower and upper tolerances determines the minimum and maximum values of V_{out} .

Given the upper and lower tolerances, we will now generate two parameters sets that describe the worst case behaviour.

For each component, the sign of the partial derivative determines if a parameter set contains the lower
lower_tol := data[.., 3] upper_tol := data[.., 4]

If a component's partial derivative is positive, multiply the nominal value by the lower tolerance (or the upper tolerance otherwise)

```
pars_1 := [seq(varNames[i] = varValues[i] · (1 + ifelse(derivs[i] > 0, lower_tol[i], upper_tol[i])), i = 1..12)]
```

If a component's partial derivative is positive, multiply the nominal value by the upper tolerance (or the lower tolerance otherwise)

```
pars_2 := [seq(varNames[i] = varValues[i] · (1 + ifelse(derivs[i] > 0, upper_tol[i], lower_tol[i])), i = 1..12)]
```


DC Response

Set $s = 0$ to calculate the DC response over a range of V_{in}

```
p1 := plot(eval(Vout, [pars_1[ ], s=0]), Vin=-5..5, color=black)
```

```
p2 := plot(eval(Vout, [pars_2[ ], s=0]), Vin=-5..5, color="DarkRed")
```
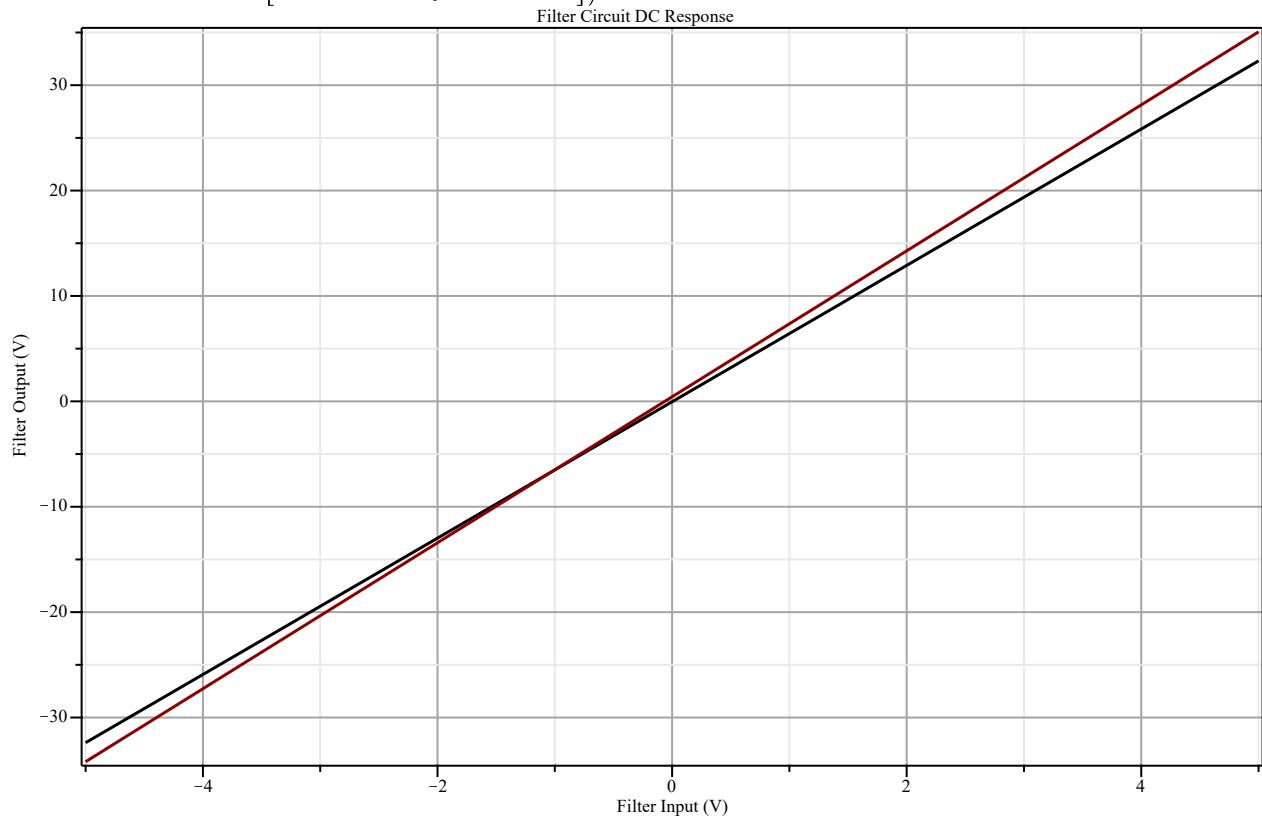
```
plots:-display(p1, p2, axes=box, gridlines, title = "Filter Circuit DC Response",
labels = ["Filter Input (V)", "Filter Output (V)"],
labelfirections=[horizontal, vertical]) =
```



Steady-state Response at 1.5 kHz


```
p1 := plot(ifelse(Vin<0, -1, 1)·abs(eval(Vout, [pars_1[ ], s=2·π·1 i·1500])), Vin=-5..5, color=black)
```

```
p2 := plot(ifelse(Vin<0, -1, 1)·abs(eval(Vout, [pars_2[ ], s=2·π·1 i·1500])), Vin=-5..5, color="DarkRed")
```

```

plots:-display(p1, p2, color = red, axes = box, gridlines,
  title = "Filter Steady State Response",
  labels = ["Filter Input (V)", "Filter Output (V)"],
  labeldirections = [horizontal, vertical]) =

```

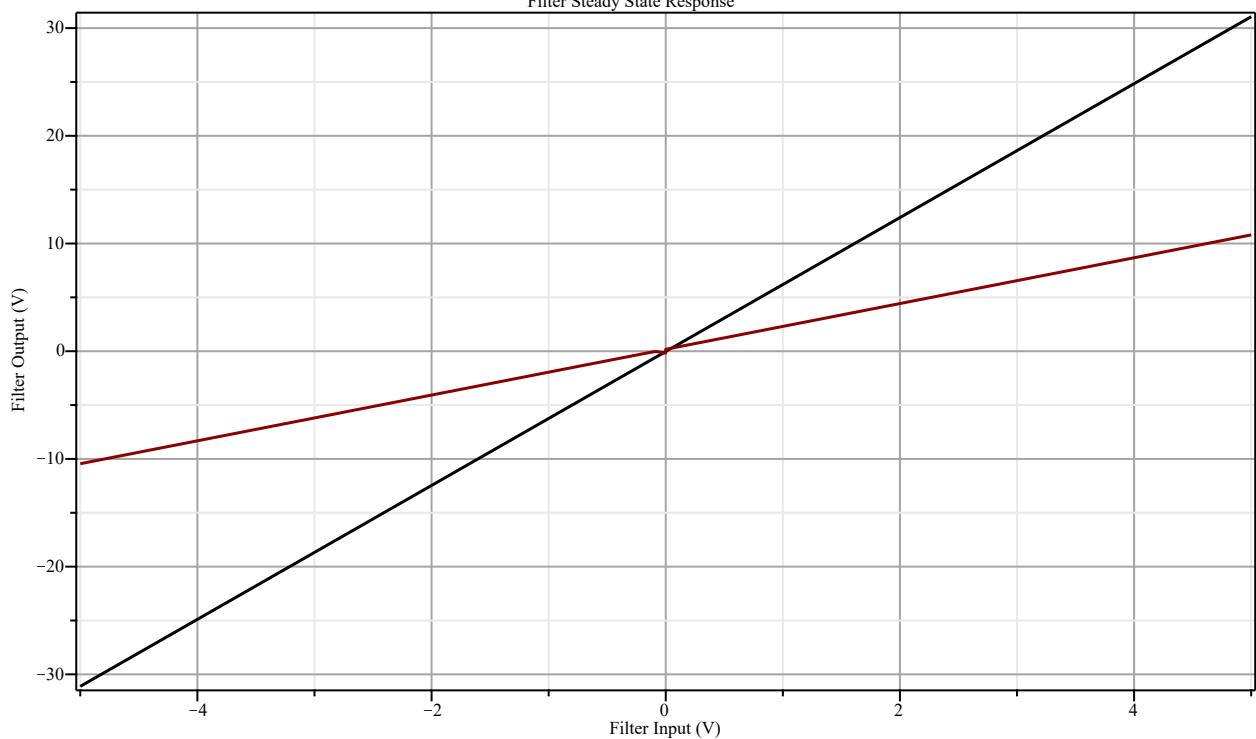

Cutoff Frequency

A magnitude plot demonstrates how the cutoff frequency varies with the two worst case parameter sets

$$tf := \text{DynamicSystems}:-\text{TransferFunction}\left(\frac{V_{\text{out}}}{V_{\text{in}}}\right)$$

```

p1 := DynamicSystems:-MagnitudePlot(tf, parameters = [pars_1[ ], V_in = 5], range = 10 .. 10^4,
hertz, color = black)

```

```

p2 := DynamicSystems:-MagnitudePlot(tf, parameters = [pars_2[ ], V_in = 5], range = 10 .. 10^4,
hertz, color = "DarkRed")

```

```
plots:-display(p1, p2, title = "Filter Frequency Response") =
```

