

Three Phase Meter

Introduction

A friend has a lathe with a 3 phase motor and lives in a country area with only a 1 phase supply. Provision of a 3 phase supply was prohibitive. So he bought a device that converts a single phase mains supply to 3 phases. However, it needs manual adjustment of the phase angle when under load. So he asked me to design and build a phase meter for him.

Circuit Description


The 3 phase mains are even more dangerous than the single phase since there is 415 Volt between the phases. Thus a safe isolation unit is required between the mains and the low voltage section. This isolation is provided by Opto Couplers OP1, OP2 and OP3.



The 3 phase signals from the Opto Couplers are squared by the Schmitt triggers IC1a, b & c and then applied to the exclusive OR gates IC5a & b via IC4. The output of the exclusive OR gates is a square wave signal whose mark to space ratio is proportional to the phase difference. These signals are applied to the averaging amplifiers IC6a & b. Diodes D4 & D5 prevent a reverse current through the meters if the phase angle is less than 90° . NB. the exclusive OR gates cannot determine the sign of the phase angle, ie. -120° will result in the same waveform as $+120^\circ$. Hence IC3a & b are employed to detect the sign. When S2 is open, IC5c inverts the IC4/10 signal so that the D Types are clocked on the negative edge of this signal. Hence if the sign of the phase is correct, O₅ will go Low and O₆ High thus illuminating the LEDs. See Figure 5.

In order to calibrate the meters, IC2a is configured as 3 stage Twisted Ring Counter which generates a 3 phase test waveform. Refer to Figure 4. Note that the phase difference between O₁, O₂ and O₃ is 60° but since O₂ is inverted by IC5d, the correct phase differences (120°) are obtained. See Figure 5.

The power on reset is generated by IC1f. This necessary because the counter could start in state 010 or 101. If so, the counter would oscillate between these states rather than count in the correct sequence.

When S1 is set to the Test position, IC4 switches the test waveforms to IC5a, 5b & 5c. The meters are calibrated by adjusting RV2 & RV3 to set the meters to centre scale (0.5 mA which represents 120°) and both LEDs should be lit indicating that the sign of the phase is correct. If switch S2 is closed while S1 is in the test position, IC5c inverts the phase of the clock signal to IC3a & 3b thus extinguishing the LEDs.

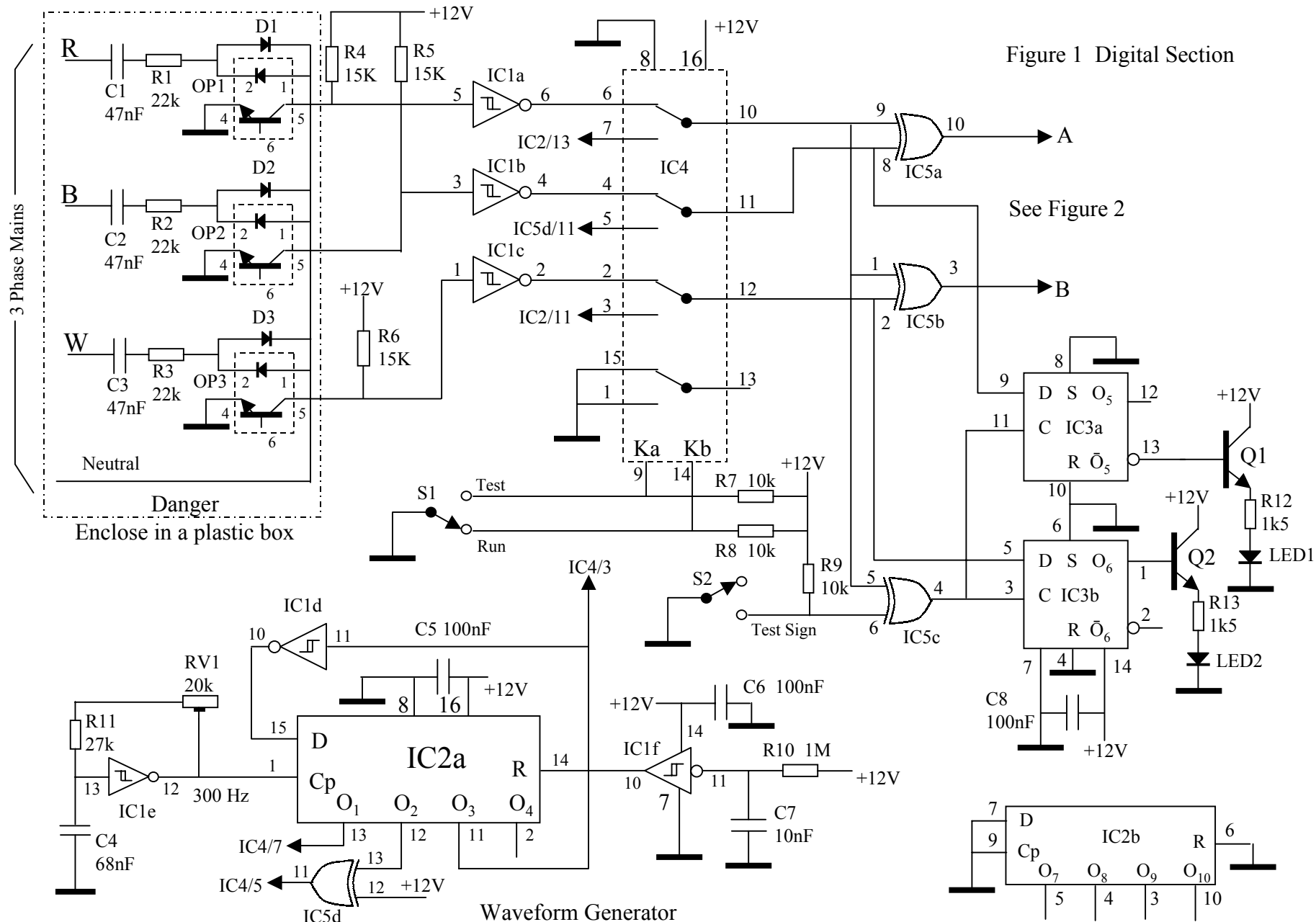

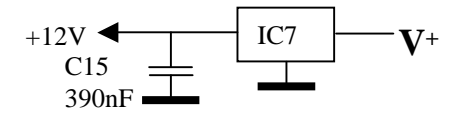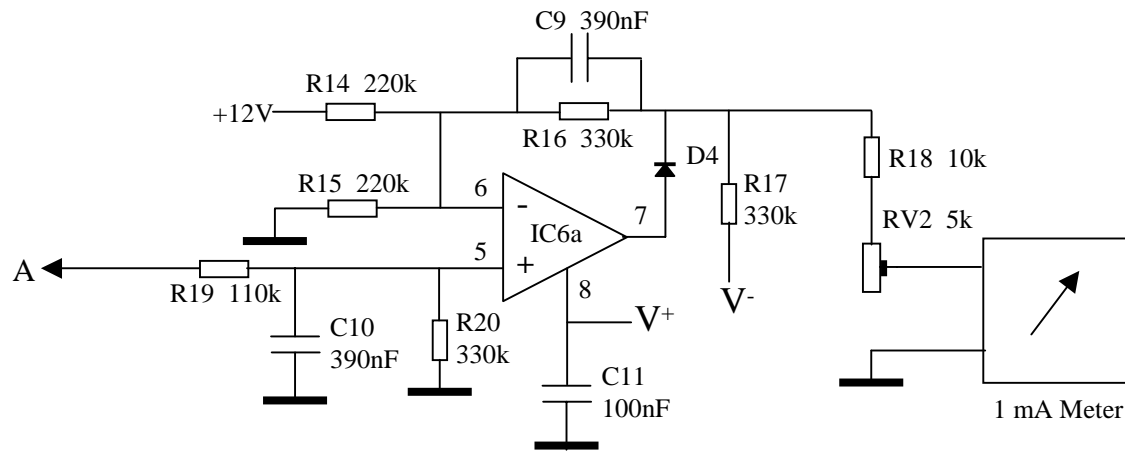

V^+ & V^- are unregulated
 $V^+ = 15 \sim 20$ Volt
 $V^- = -7 \sim -12$ Volt

See Figure 1

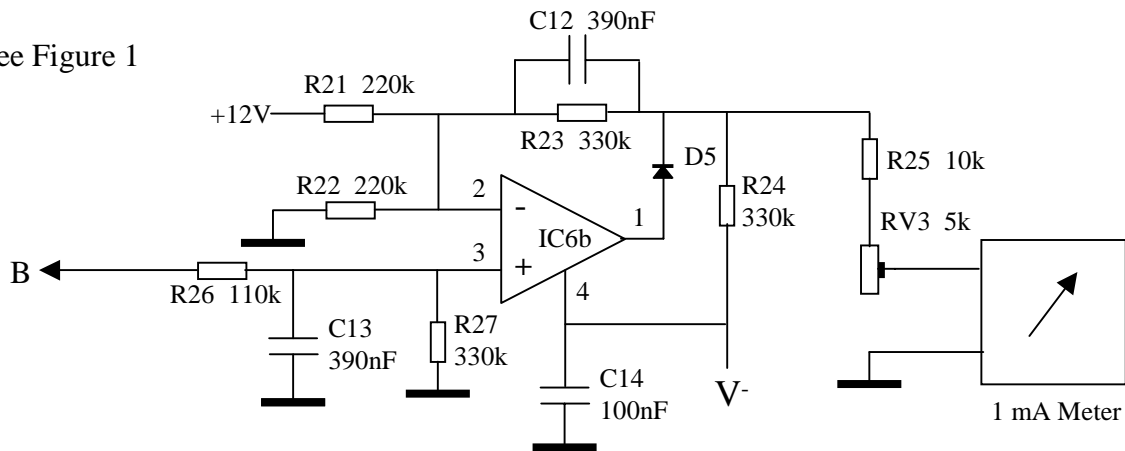


Figure 2 Analogue Section

O ₁	O ₂	O ₃
0	0	0
1	0	0
1	1	0
1	1	1
0	1	1
0	0	1

Figure 3 Count Sequence

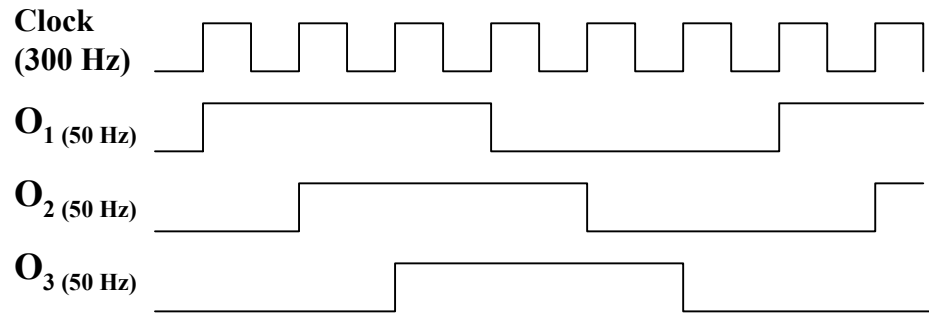


Figure 4 Waveforms of Twisted Ring Counter

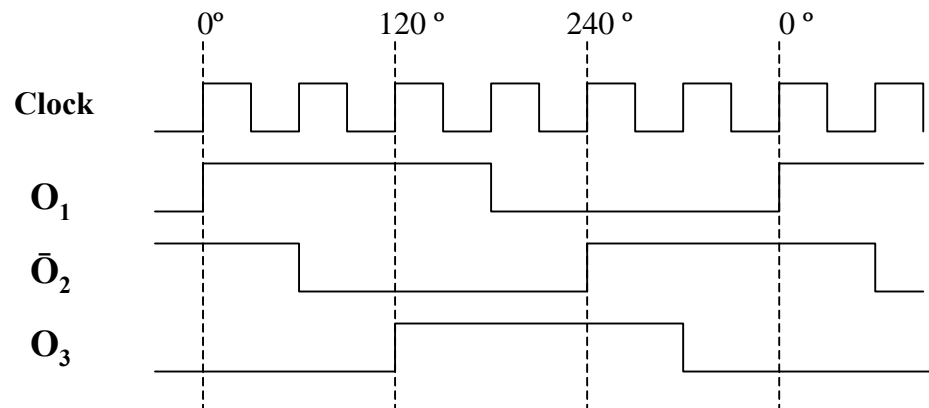


Figure 5 Waveforms Showing O₂ inverted & phase angle

Parts List

OP1, 2, 3

IC1

IC2

IC3

IC4

IC5

IC6

IC7

C1, 2, 3

C4

C5, 6, 7, 8

C9, 10, 12, 13

C11, 14

R1, 2, 3

R14, 15, 21, 22

R16, 20, 23, 27

R19, 26

All other resistors are ¼ Watt, 5%

D1, 2, 3, 4, 5

Q1, Q2

RV1

RV2, 3

4N25 Opto Coupler

40106 Hex Schmitt Trigger

4015 Dual 4 Bit Shift Register

4013 Dual D Type Flip Flop

4019 Quad 2 input Multiplexer

4030 Quad Exclusive OR gate

LF353 Dual Op Amp

78L12 Voltage Regulator

47 nF Capacitor 250 V Mains rated

68 nF 50 Volt

100 nF 50 Volt ceramic

390 nF 50 Volt ceramic

100 nF 50 Volt ceramic

22 k ½ Watt 5%

220 k ¼ Watt, 1%

330 k ¼ Watt, 1%

110 k ¼ Watt, 1%

1N4148

PN100

20 k Trim pot

5 k Trim pot