

## Unijunction Transistor (Volt-Ampere Characteristics)

**Aim** :- To draw the volt-ampere characteristics of the unijunction transistor and to find the UJT parameters.

**Apparatus** :- UJT, two variable d.c. power supplies, d.c. voltmeter, d.c. milli-ammeter, multi-meter and connecting terminals.

**Formulae** :- 1. Peak point voltage =  $V_P$  (V) (From the graph)

2. Valley point voltage =  $V_V$  (V) (From the graph)

3. Intrinsic stand off ratio  $\eta = \frac{V_P - V_B}{V_{BB}}$

Where  $V_B$  = Barrier potential of P-n junction of Silicon diode = 0.7V

$V_{BB}$  = Voltage applied between two bases  $B_1$  and  $B_2$  (V)

4.  $R_{B1} = \eta R_{BB} \quad \therefore \eta = \frac{R_{B1}}{R_{BB}} = \frac{R_{B1}}{R_{B1} + R_{B2}}$

$R_{BB}$  = Inter base resistance ( $\Omega$ )

5.  $R_{B2} = R_{BB} - R_{B1}$

6. Negative resistance = Slope of V-I curve in the negative resistance region.

OR  $\frac{dV_E}{dI_E} = \frac{AB}{BC}$

7. Switching efficiency =  $V_P - V_V$

**Description** :- In UJT a Silicon bar is taken and it is lightly doped with V- group material. So the silicon bar acts as lightly doped n – material and on one side of the bar above center a small region is heavily doped with III – group element Which then acts as P – material. Some times instead of doping with 3<sup>rd</sup> group element a Aluminum wire is made contact at that region and that region acts as P- material. At the two ends of n – type material two wires are connected with ohmic contact, these two terminals are called “Bases” (  $B_1$ - lower and  $B_2$  - upper ) and another wire for the P – region is connected and is called “Emitter” (E). The UJT is as shown in Fig. 1

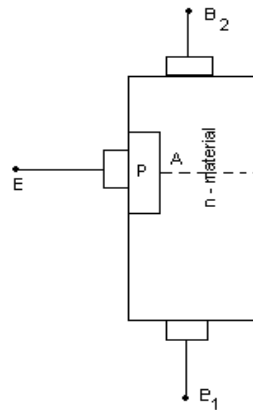


Fig. 1

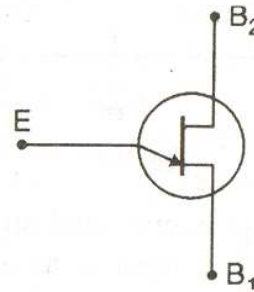


Fig. 2

Since the Silicon bar is lightly doped, the resistance between the bases  $B_2$  and  $B_1$  is high and its value ranges from  $5\text{ K}\Omega$  to  $10\text{ K}\Omega$  at room temperature. This is called 'double base diode'. If some potential is applied between the bases  $B_2$  and  $B_1$ , a uniform potential gradient is developed between them. Because of its resistance this will also acts as a potential divider and this divides the potential at  $E$ . In this UJT it has only one P-n junction, so it is called unijunction transistor. ( Since it has three terminals it acts as transistor.)

The circuit symbol of UJT is as shown in the fig. 2. The arrowed terminal is the emitter and it gives the conventional current direction. The emitter arrow is inclined towards the base  $B_1$  terminal because in the 'conducting state' the current will flow from emitter to base  $B_1$ .

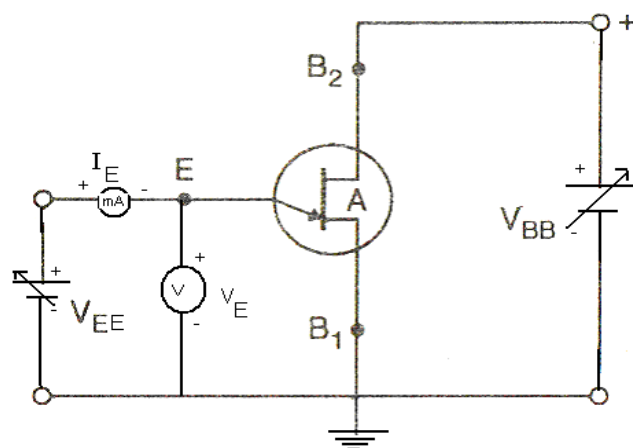


Fig. 3

**THEORY** :- Case 1:- First the emitter (E) is open i.e. it is given zero potential and a fixed voltage ' $V_{BB}$ ' is applied between two bases  $B_1$  and  $B_2$ , such that  $B_2$  is given positive that is  $B_2$  is at  $+V_{BB}$  and  $B_1$  is at zero potential. This  $V_{BB}$  produces a current from  $B_2$  to  $B_1$ , which in turn produces a uniform potential gradient between  $B_2$  and  $B_1$ , as the Silicon bar has a resistance of 5 K $\Omega$  to 10 K $\Omega$ .

The potential at the point 'A' in the Silicon bar, where the emitter region touches the n-type bar is ' $\eta V_{BB}$ ', where  $\eta$  is the intrinsic stand off ratio or 'voltage division factor'. The emitter is open means it is given zero potential then the P-n junction is reverse biased, and the current through the junction is zero.

Case 2:- Now a variable voltage  $V_E$  from a source  $V_{EE}$  is applied between the emitter E and base  $B_1$ . When  $V_E$  is less than ' $\eta V_{BB}$ ' then the P-n junction is reverse biased and the resistance between A and  $B_1$  i.e.  $R_{B1}$  is high. In this stage a small reverse leakage current will flow  $B_2$  to E.

When  $V_E$  exceeds  $\eta V_{BB}$  then the junction is forward biased, but when  $V_E \geq \eta V_{BB} + V_B$ , holes enter from emitter 'E' to the n-type bar and these are repelled by the base  $B_2$  due to its positive potential and are attracted by  $B_1$  which is at negative potential. (Actually these holes get neutralized by attracting electrons from  $B_1$ , here  $V_B$  is the potential barrier of P-n junction). So the conductivity of this part of bar (A to  $B_1$ ) increases and the resistance  $R_{B1}$  decreases. i.e. The emitter current  $I_E$  causes a decrease in the resistance which is known as negative resistance characteristic. In this stage emitter voltage  $V_E$  also decreases to a low value corresponding to the decrease of resistance  $R_{B1}$ . This minimum voltage is called the 'valley point voltage'  $V_V$  and the corresponding current is called 'valley point current'  $I_V$ . The emitter voltage is maximum when  $V_E = \eta V_{BB} + V_B$  and is called 'peak point' voltage ( $V_P$ ) or 'firing potential'. The current corresponding to  $V_P$  is called 'peak point current'  $I_P$ . Above  $I_V$  the  $V_E$  increases gradually and this state is called 'on-state' and the corresponding region in the graph is called 'saturation region'.

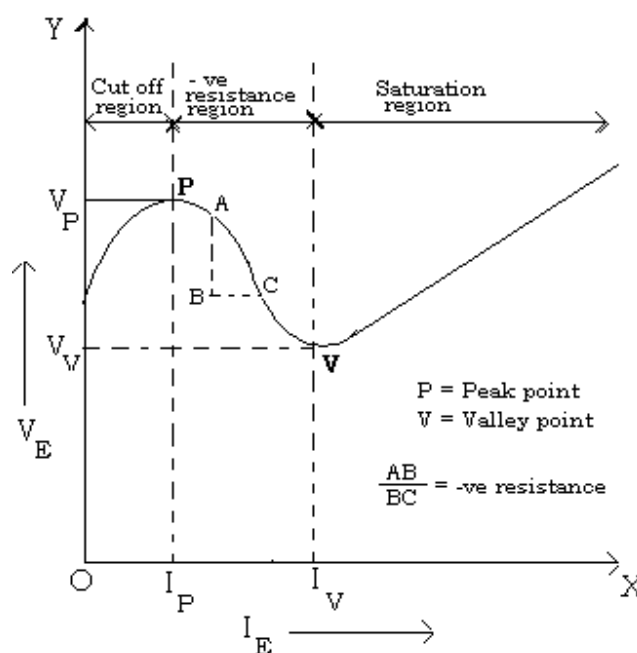


Fig. 4

**Procedure** :- First the emitter is open and the inter base resistance ' $R_{BB}$ ' is measured with a ohmmeter. Now the circuit is connected as shown in Fig.3. Apply a fixed voltage  $V_{BB}$  (5V to 10V) between the two bases  $B_1$  and  $B_2$ . Increase the emitter voltage  $V_E$  in convenient steps starting from zero. Note the corresponding emitter current  $I_E$ . Draw a graph by taking  $I_E$  on X-axis and  $V_E$  on Y-axis. The shape of the graph is as shown in the Fig. 4. Note the peak point P and valley point V also note the corresponding voltages  $V_P$  &  $V_V$  and currents  $I_P$  &  $I_V$ . Find the value of intrinsic stand off ratio  $\eta$ , switching efficiency  $(V_P - V_V)$ ,  $R_{B1}$  and  $R_{B2}$  using the above formulae. Also find the value of the negative resistance of UJT from the slope drawn to the curve in the -ve resistance region.

The characteristic curves can be drawn with different values of  $V_{BB}$ . The  $V_P$  and  $V_V$  values increase with the increasing value of  $V_{BB}$ . The  $I_P$  and  $I_V$  values do not change with the change of  $V_{BB}$ . The switching efficiency also increases with increasing value of  $V_{BB}$ .

**Graph-1** :- A graph is drawn by taking emitter current  $I_E$  on X-axis and emitter Voltage  $V_E$  on Y-axis. From the graph the  $V_P$  and  $V_V$  values and  $I_P$  and  $I_V$  values are noted as shown in the graph Fig. 4.

**Precautions** :- 1) The continuity of the connecting terminals should be checked before going to connect the circuit.

2) Identify the two bases and emitter of UJT and connect properly.

3) The power supply should be 'on' only when the observations are taken.

---

### **Table**

| S. No. | $V_{BB} =$ Volt |              | $V_{BB} =$ Volt |              |
|--------|-----------------|--------------|-----------------|--------------|
|        | $I_E$ (mA)      | $V_E$ (Volt) | $I_E$ (mA)      | $V_E$ (Volt) |
|        |                 |              |                 |              |

\* \* \* \* \*